



AMERICAN INTERNATIONAL UNIVERSITY – BANGLADESH (AIUB)

Where leaders are created

Course Code: EEE 2104 **Course Name:** Digital logic and circuit Lab

Remote control circuit through RF without microcontroller

Course Teacher: S M Tanvir Hassan Shovon

Professor

Department of Electrical and Electronic Engineering

SL #	Students ID	Students Name	Program	Section
1	23-50518-1	Zifanur Rahman turjo	BSc in CSE	D
2	23-50536-1	Rashedul alam	BSc in CSE	D
3	23-50540-1	Kallol dey	BSc in CSE	D
4	23-50558-1	Sumya bristy	BSc in CSE	D
5	23-50633-1	Numan nur helaly	BSc in CSE	D

Objectives of the Work

- Design a remote control system using RF **without** a microcontroller.
- Utilize **HT12E** and **HT12D** encoder-decoder pair.
- Ensure cost-effective and efficient wireless communication.
- Enable simple implementation for automation and security systems.
- Maintain low power consumption with reliable operation.

Introduction

- **Wireless communication enables modern electronics to operate remotely.**
- **RF systems replace traditional wired control with flexibility and simplicity.**
- **Motivation:**
 - **Avoid complexity of microcontrollers.**
 - **Build a cost-effective wireless control system.**
- **Applications in home automation, security, and industry.**

Literature Review

- RF-based systems are widely used in consumer and industrial electronics.
- Many systems use microcontrollers (complexity and cost).
- **Our work eliminates microcontroller:**
 - Simplifies design.
 - Reduces power and cost.
- HT12E/HT12D pair used in previous basic RF applications.

Working Method

- **HT12E (Encoder) + 433MHz Transmitter**
 - The **HT12E** takes **4-bit parallel data** and encodes it into a **serial** signal.
 - The **433MHz Transmitter** sends this serial data wirelessly.
- **433MHz Receiver + HT12D (Decoder)**
 - The **433MHz Receiver** gets the **serial** data.
 - The **HT12D** decodes it and converts it back to **4-bit parallel data**.

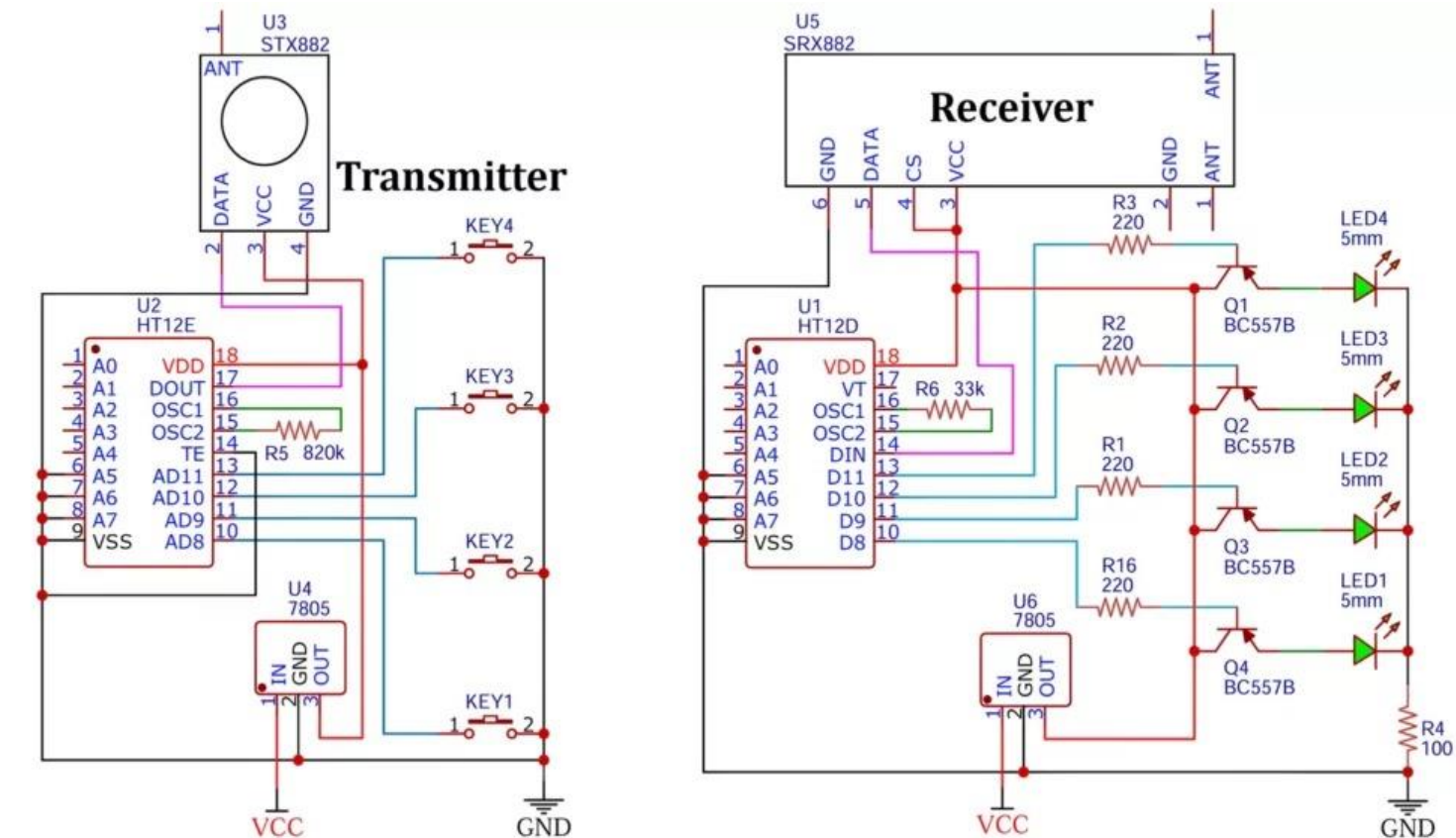


Fig 1: Circuit Diagram

Working Method

- Built on breadboard
- Transmitter powered by 5V supply.
- Receiver connected to LED/relay for action.
- **Components:**
 - RF Modules: STX882/SRX882
 - Encoder/Decoder: HT12E/HT12D
 - Resistors, Transistors, Voltage Regulator, Push Buttons, LEDs

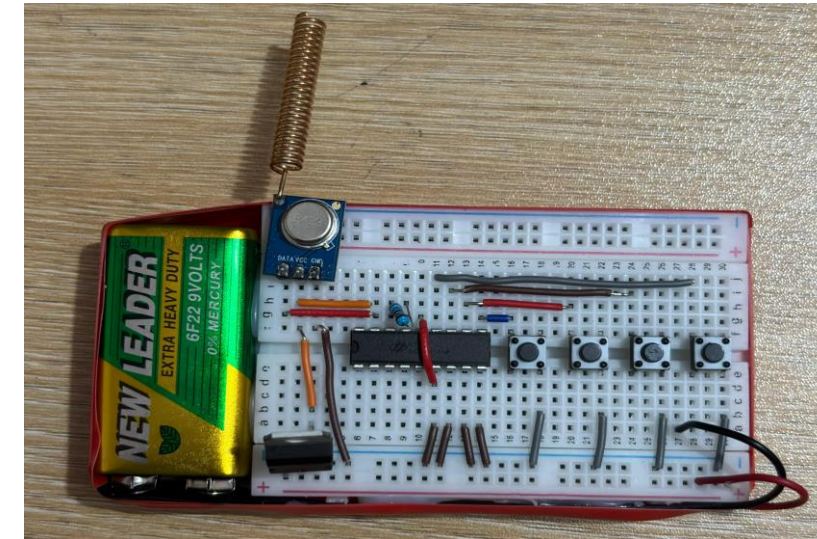


Fig 2: Transmitter circuit

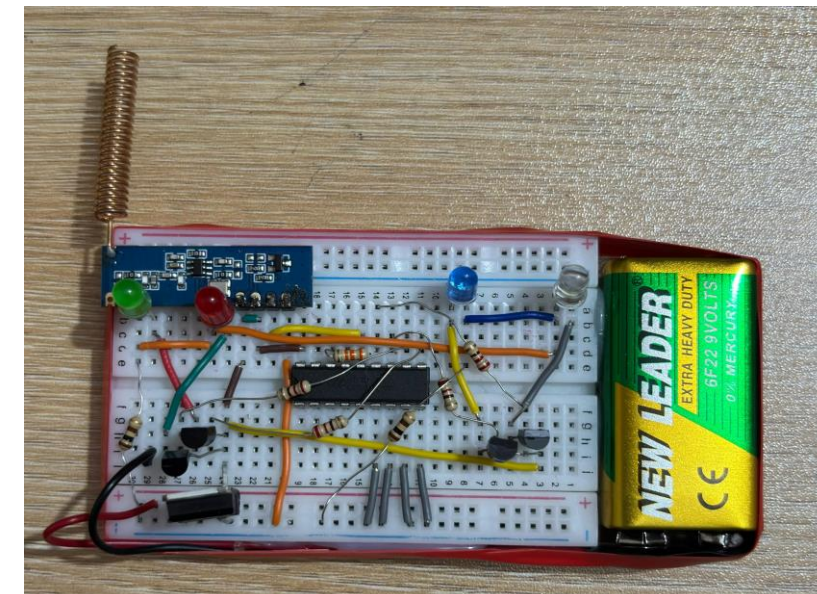


Fig 3: Receiver circuit

Here is a video how it works



Result and discussion

- Pressing transmitter buttons successfully triggers receiver output.
- LED lights indicate correct signal reception.
- Can operate over a range of 100 meters.
- Consumes minimal power, ideal for battery applications.
- Stable communication with minimal interference.

Applications

- Remote control(Toys, Garage doors, Fans, Lights)
- Wireless security systems
- Home Automation
- Doorbells
- Short-range data transmission
- Remote control of household appliances

Advantage

- Wireless and flexible device control.
- Controls up to four devices.
- Uses low-cost, easy-to-find parts.
- Low power usage.
- Simple and easy to build.

Disadvantage

- Potential Interference:** RF signals are susceptible to interference from other electronic devices and physical obstructions, which can affect performance.
- Security Concerns:** Hackers can intercept signals without proper encoding, creating security risks in sensitive applications.
- Limited Range:** Obstacles and interference can reduce the circuit's effective range.

Conclusions

Building a 433MHz RF transmitter and receiver circuit is an excellent way to explore wireless communication. With a simple design and affordable components, this circuit offers a reliable solution for remote control applications.

Thanks for listening our presentation....

