

# Remote Control Circuit through RF without Microcontroller

**Rashedul alam**

Dept. of Computer Science  
Engineering

[23-50536-1@student.aiub.edu](mailto:23-50536-1@student.aiub.edu)

**Zifanur rahman turjo**

Dept. of Computer Science  
Engineering

[23-50518-1@student.aiub.edu](mailto:23-50518-1@student.aiub.edu)

**Kallol dey**

Dept. of Computer Science  
Engineering

[23-50540-1@student.aiub.edu](mailto:23-50540-1@student.aiub.edu)

**Sumya afroz bristy**

Dept. of Computer Science  
Engineering

[23-50558-1@student.aiub.edu](mailto:23-50558-1@student.aiub.edu)

**Numan nur helaly**

Dept. of Computer Science  
Engineering

[23-50633-1@student.aiub.edu](mailto:23-50633-1@student.aiub.edu)

**Supervised by -**

S.M Tanvir hassan Shovon  
Section - D  
Group - 6

**Abstract—** Wireless technology has uncommonly changed how electronic devices communicate and operate. This project shows a simple remote control circuit that uses RF transmission without needing a microcontroller. An RF transmitter and receiver module are used along with an encoder-decoder pair HT12E and HT12D to allow wireless communication. Users can control devices remotely by simply pressing specified push buttons, eliminating the need to interface with microcontroller programming. The main features of this system are its low cost, simplicity of design, and reliability. Several applications include home automation, remote-controlled lighting, security systems, and industrial operations which require wireless control. The system is designed to consume low power with stable communication to provide an effective solution for remote controlled systems.

**Keywords—** Radio Frequency, Transmitter, Receiver, 433 MHz, Antenna.

## 1. Introduction

Remote control devices form an important part of daily life enhancing the convenience in using electronic appliances such as televisions and radios. The development of microcontroller based devices has opened a new era in sophisticated remote controls systems simplifying the entire requirement of remote control system. The project described herein is an attempt to develop an RF based remote control circuit that does not utilize a microcontroller.

The first part of this project focuses on developing the transmitter part which is the most important unit of the remote control. The encoder encodes all buttons and this encoded information is then sent to an RF transmitter module. On the second part we focus on the counter part of the remote the receiver. The basic function of the receiver is to handle incoming data and then send the output into a designated power section where the output becomes a specific instruction that is sent to the details section of the power. By combining a simple RF control with two sections, users can enjoy a functional, affordable, and easy to use remote controlled worker. Since this project can be used for beginners who are interested in digital electronics, this would make a great addition to their learning resources.

### 1. Project Objectives

The primary objectives of this project are:

Create RF communication-based remote control Circuit without microcontrollers. Control wireless devices using RF transmitters, receivers, and decoders/encoders. Design simple and cost-effective remote control systems. Build an uncomplicated yet dependable automation, security and industrial systems.

### 2. Components

1. RF Transmitter Module (STX882)
2. RF Receiver Module (SRX882)
3. HT12E Encoder IC
4. HT12D Decoder IC
5. Push Buttons
6. LEDs (for output indication)
7. Resistors (220 $\Omega$ , 33k $\Omega$ , 820k $\Omega$ , 100k $\Omega$  etc.)
8. Transistors (BC557B)
9. Voltage Regulator (7805)
10. Power Supply (5V)

### 3. Circuit Diagram

The circuit consists of two main parts: the transmitter and the receiver. The transmitter section includes an RF module connected to the HT12E encoder IC, which takes input from push buttons and transmits encoded signals. The receiver section consists of an

RF receiver module and an HT12D decoder, which decodes the signals and activates corresponding outputs. The circuit diagram is shown below.

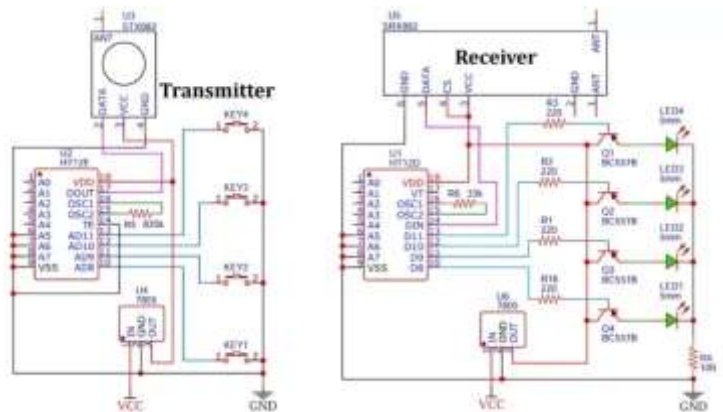


Fig. 3. Circuit Diagram

### 4. Working Principle

1. The HT12E encoder makes a serial code for every button pressed on the transmitter.
2. The encoder sends the encoded signal wirelessly through the RF transmitter (STX882).
3. The captured signal from the RF transmitter is sent to the HT12D decoder via the SRX882 RF receiver.
4. After receiving the signal, the HT12D decoder checks if the signal is valid and attempts to decode it, if successful, gives parallel output.
5. The signal that is decoded determines what should be done next which can include flashing an LED or energizing a relay.
6. When connected to a relay, it is possible to control devices such as fans, lights or even security alarms.
7. For remote control applications, the system guarantees responsive action and dependable results.

## 5. Hardware Implementation

. For the implementation of the project, it is required to mount the Transmitter and receiver circuits on either a PCB or a breadboard. The transmitter part is incorporated of push buttons which are connected to an HT12E encoder IC that has been interfaced with the RF transmitter module. A power supply of 5V is supplied to guarantee proper functioning. The receiver part consists of the RF receiver module as well as an HT12D decoder IC which decodes the signal to control the output devices connected such as relays or LED's. The system is tested by pressing such buttons on the transmitter and observing the signal reception and transmission.

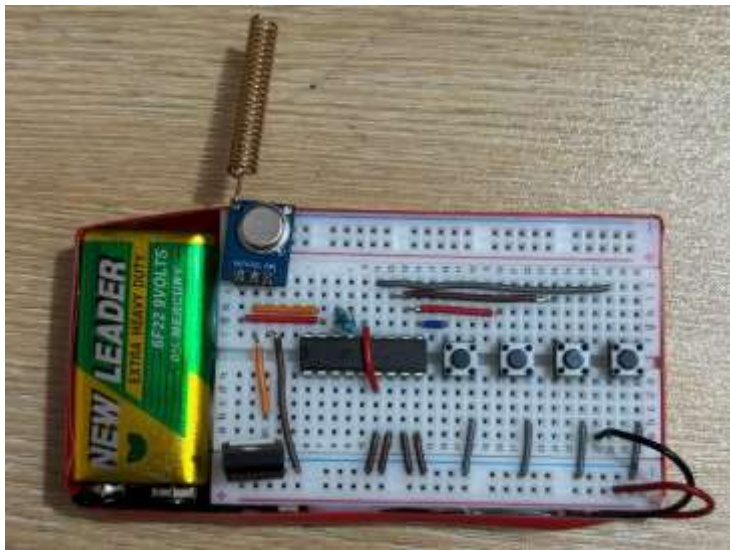


Fig. 2. Transmission Circuit

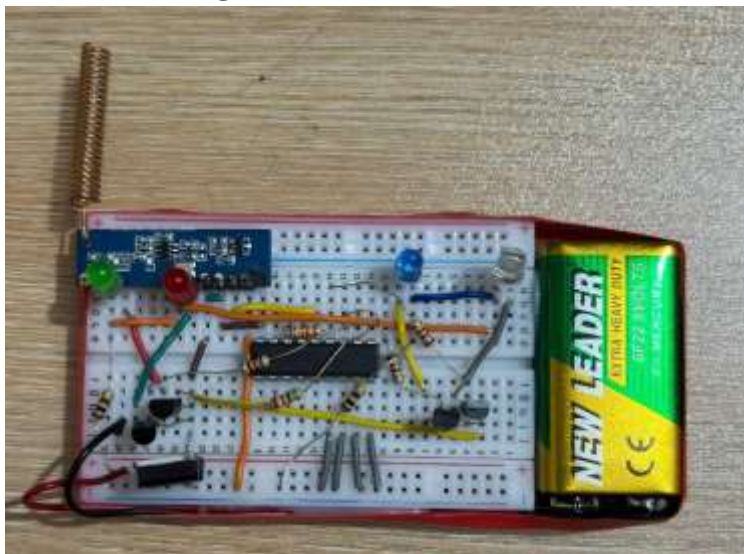


Fig. 3. Receiver Circuit

## 6. Applications & Advantages

### 6.1 Applications:

1. **Home Automation Systems:** Can remotely operate household devices such as lights and fans
2. **Wireless Lighting Control :** Remote access lighting control enables turning lights on and off
3. **Remote-Controlled Door Locks:** Allows for enhancing security by locking and unlocking door wirelessly.
4. **Industrial Remote Operations:** Aiding in improving efficiency and safety by remote control of machinery and equipment.
5. **Security Systems:** Can be set for remote surveillance to provide enhanced safety, alarm ac

### 6.2 Advantages:

1. **Simple and Cost-Effective:** Lacks complex programming requirements by easily available components.
2. **No Need for Microcontroller Programming:** Removal of coding makes it easy for non-programmers to access.
3. **Reliable RF Communication:** Useful in spatially limited distances for effective wireless communication.
4. **Low Power Consumption:** Adequate for battery-operated functionalities, the system is energy efficient.
5. **Scalability:** Increased remote control functions can be added without difficulty.
6. **User-Friendly Design:** Every user can appreciate the ease of circumventing simple button functions.

## **7. Results & Conclusion**

This project demonstrates a complete wireless remote control system using RF technology without any microcontroller involvement. Controlling devices remotely was made possible using an RF transmitter and receiver with an encoder-decoder pair. This system is easy and inexpensive which makes it a superb project for beginners in digital electronics and wireless communications. Also, the addition of relays makes it possible to control high-power appliances, increasing its practical usefulness. It may also be developed further by increasing the number of channels for multi-device control and improving signal privacy to prevent unauthorized access.

## **8. Reference**

- [1] Datasheets of HT12E and HT12D ICs
- [2] RF module datasheet (STX882 & SRX882)
- [3] Online resources on RF communication